



DEPARTMENT OF ELECTRONICS AND TELECOMMUNICATION ENGINEERING
CHITTAGONG UNIVERSITY OF ENGINEERING AND TECHNOLOGY
CHATTOGRAM – 4349, BANGLADESH

Experiment No. 3

Design and Performance Analysis of an Inverter Using Cadence Virtuoso

PRECAUTIONS:

- Students must carefully read the lab manual before coming to lab to avoid any inconveniences.
- Students must carry a flash drive to transfer files and lab manuals.
- Use of mobile phone in lab is strictly prohibited and punishable offence.
- Experiment files must be uploaded to GitHub including home tasks.

OBJECTIVES:

- To familiarize with Cadence tools and library creation.
- To familiarize with inverter design and implementation.
- To familiarize with transient analysis and performance measurements.

THEORY:

Custom IC Design Flow:

Figure 1 shows the basic design flow of a custom IC design, together with the Cadence tools required in each step.

First, a schematic view of the circuit is created using Cadence Virtuoso Schematic Editor L. Then, the circuit is simulated using Cadence Analog Design Environment (ADE L). Different simulators can be employed; some sold with the Cadence software (e.g., Spectre) some from other vendors (e.g., HSPICE) if they are installed and licensed.

Once circuit specifications are fulfilled in simulation, the circuit layout is created using Virtuoso Layout Editor L. The resulting layout must verify some geometric rules dependent on the technology (design rules). For enforcing it, a Design Rule Check (DRC) is performed. Optionally, some electrical errors (e.g., shorts) can also be detected using an Electrical Rule Check (ERC). Then, the layout should be compared to the circuit schematic to ensure that the intended functionality is implemented. This can be done with a Layout Versus Schematic (LVS) check. All these verification tools are included in the Assura software in Cadence.

Finally, a netlist including all layout parasitics should be extracted using Quantus QRC tool, and a final simulation of this netlist should be made. This is called a post-Layout simulation, and is performed with the same Cadence simulation tools.

Once verified the layout functionality, the final layout is converted to a certain standard file format (GDSII, CIF, etc.) depending on the foundry using the Cadence conversion tools.

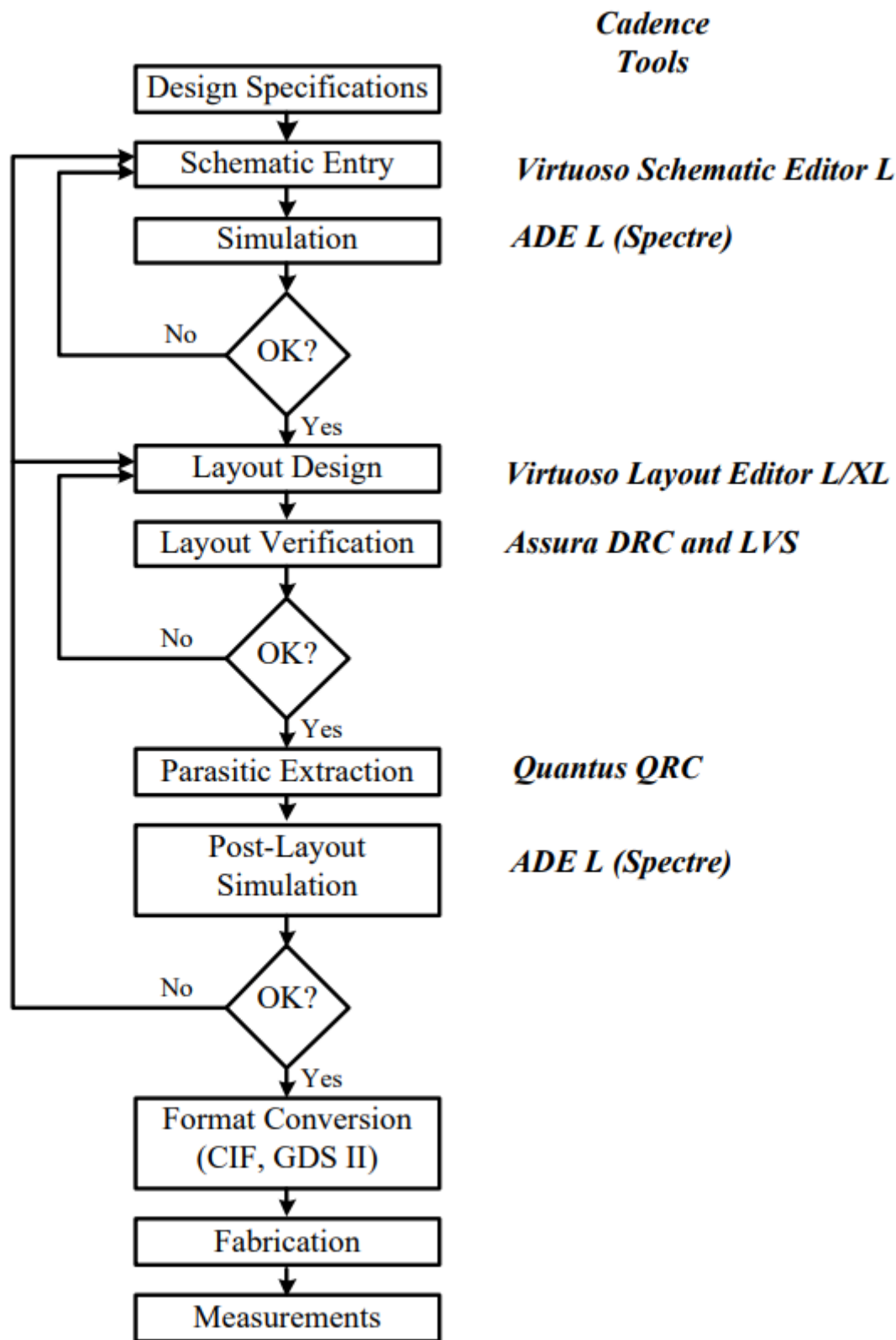


Figure 1: Flowchart of Custom IC design.

PDK:

Cadence is an Electronic Design Automation (EDA) environment that allows integrating in a single framework different applications and tools (both proprietary and from other vendors), allowing to support all the stages of IC design and verification from a single environment. These tools are completely general, supporting different fabrication technologies. When a particular technology is selected, a set of configuration and technology-related files are employed for customizing the Cadence environment. This set of files is commonly referred as a process design kit.

All VLSI designs start with a Process Design Kit known briefly as PDK. A PDK contains the process technology and needed information to do device-level design in the Cadence Design Framework II (DFII) environment.


Throughout the labs we will use a generic, foundry independent 90nm CMOS mixed-signal process kit developed by Cadence. We will call it generic PDK 90 nm briefly as gpdk090. A PDK contains all the necessary design and technology data to successfully design and simulate a VLSI

chip on a particular foundry. The foundry provides the necessary technological data, design rules, and the device models. Also, PDK contains schematic symbols with all necessary views, as well as device extraction rules for Layout versus Schematic (LVS) check. It also provides parasitic extraction rules.


DESIGN PROCESS:

Opening Cadence:

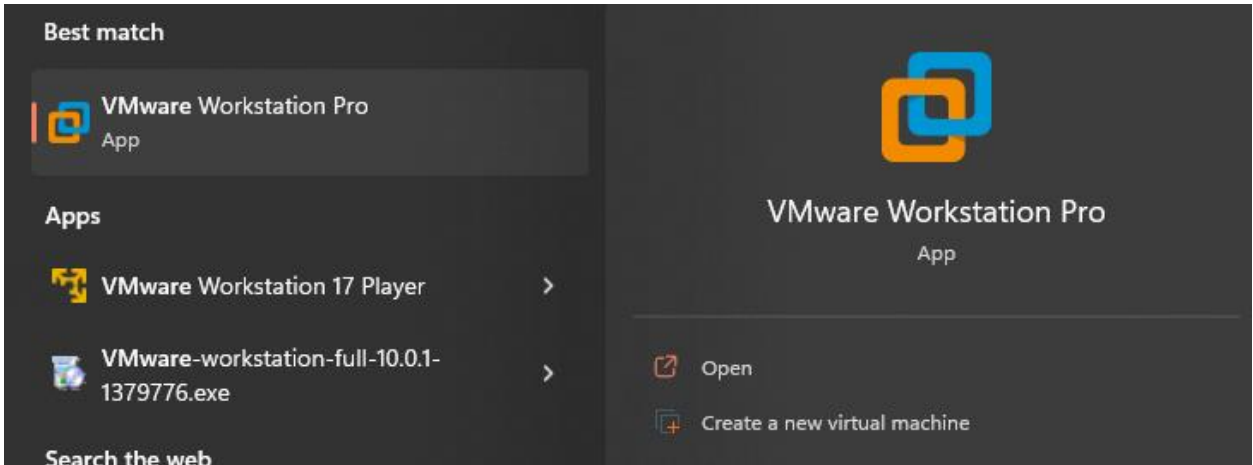
- 1. Start **VMware Workstation Pro** from the start menu.




- 2. Click **Open a Virtual Machine**.

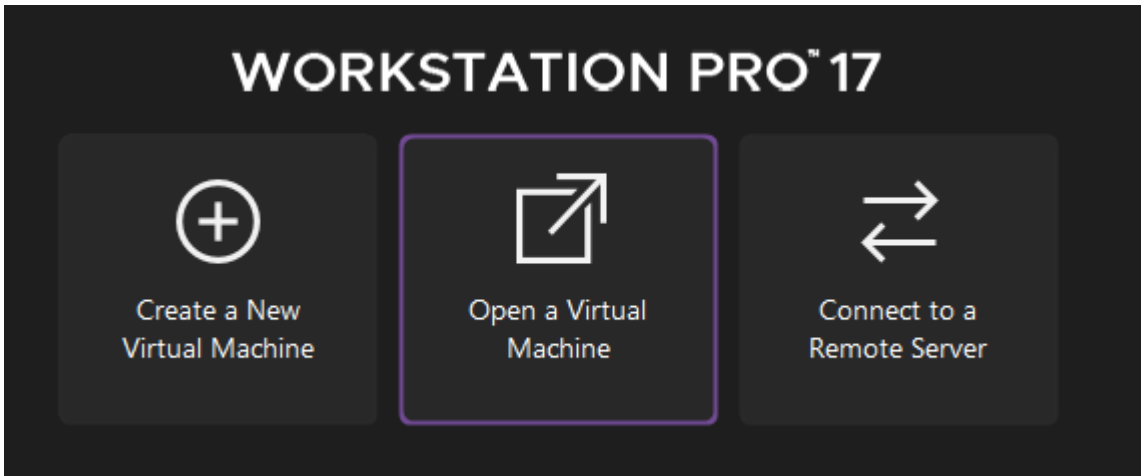

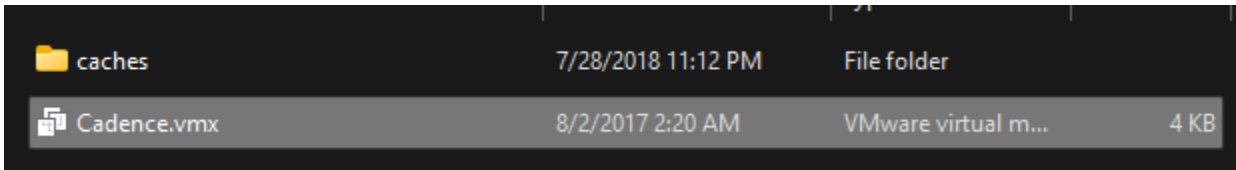- 3. Locate the **Cadence.vmx** file from your storage media.



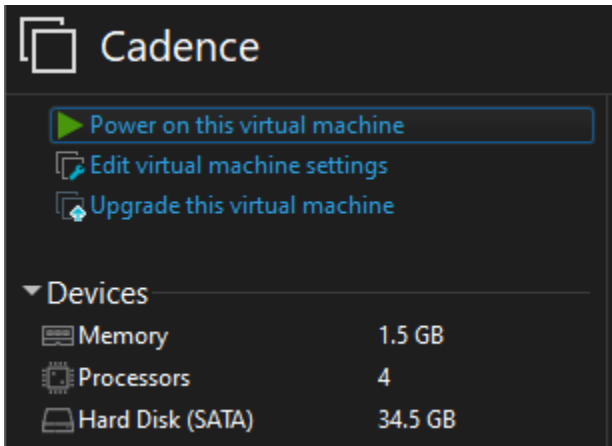- 4. Change configuration as necessary then start the VM. Click **“I Copied It”** if asked.




Starting Virtuoso:

1. Start the “**Terminal**” from the home screen.



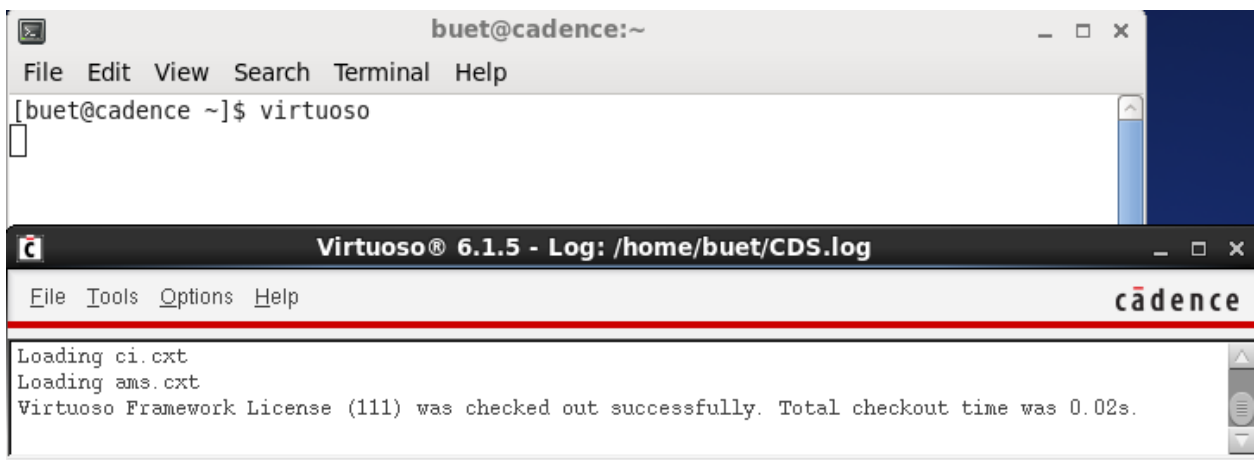2. Type in “**virtuoso**” and press enter. The **Command Interpreter Window (CIW)** will appear.



Creating and Attaching Library:


All the entities in Cadence are managed using libraries, and each library contains cells. Each cell contains different design views (the structure is similar –and physically corresponds - to a directory (library) containing subdirectories (cells), each one containing files (views). Thus, for instance, a certain circuit (e.g., an inverter) can be stored in a library, and such library can contain the different logic blocks (basic gates, flip-flops, registers, etc) stored as cells. Each block (cell) contains different views (schematic, layout, symbol, etc.).

There are usually three types of libraries:


- A set of common Cadence libraries that come with the Cadence software containing basic components, such as voltage and current sources, R, L, C, etc. (e.g., analogLib).
- Libraries that come with a certain design kit (e.g., gpdK090) and that are related to a certain technology (e.g., transistors with a certain model attached, etc.).
- User libraries; where the user stores its designs. These designs employ components from the Cadence/design kit libraries.

It is recommended that you use a library to store related cell views; e.g., use a library to hold all the cell views for a single project (that can involve a complete chip design). In our example, we are going to create a new library for our design and attach it to desired technology library.

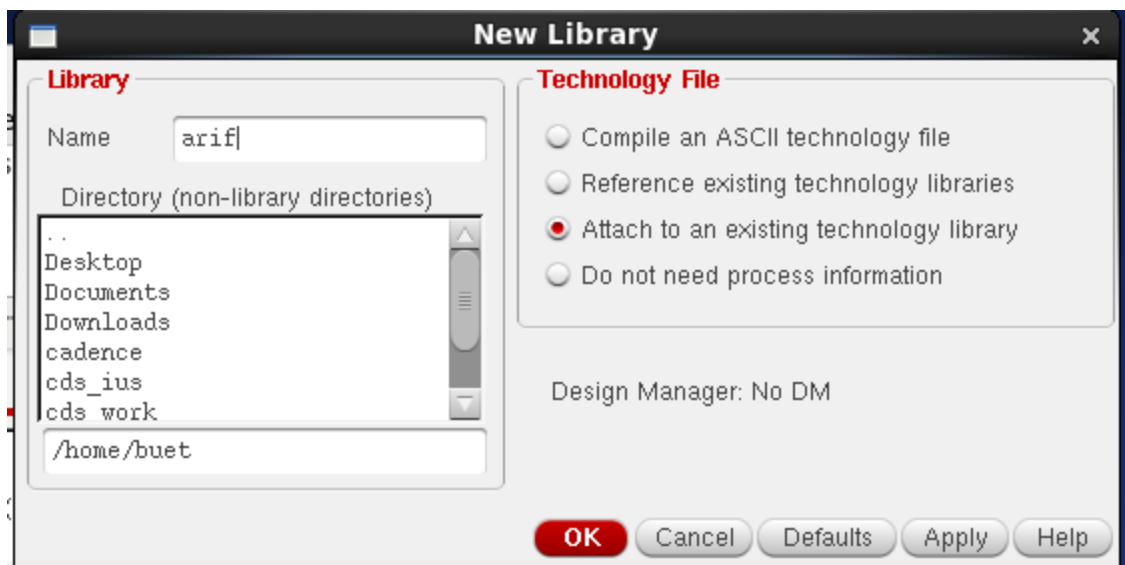1. In the **CIW**, execute **File > New > Library**.
2. The ‘**New Library**’ form appears. In the name field of the New Library type **mylib** or any name of your choice.



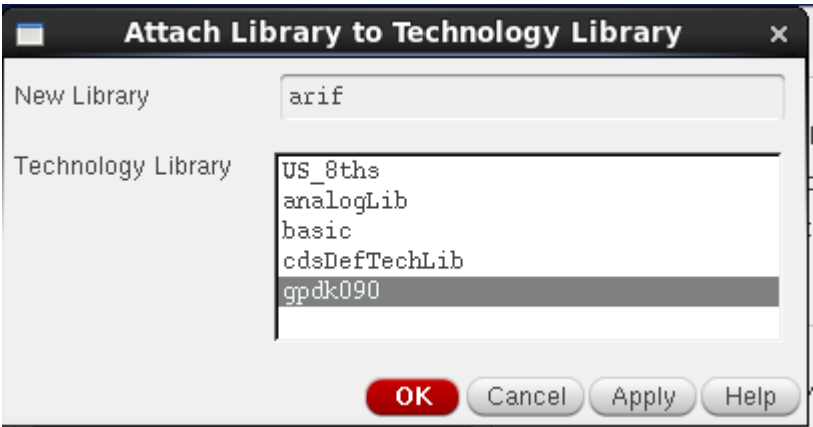3. Select **Attach to an existing technology library** and click **OK**. ‘Attach Library to Technology Library’ window will appear.




4. Select **gpdK090** technology library and click **OK**. This will be the technology chosen for your design (that you will employ eventually for fabrication). Now all the designs made in this library are technology-dependent (e.g., the schematic MOS symbols have by default the model for this technology, the available layout layers correspond to this technology, etc.).
5. The following will appear on the **CIW**.



Schematic Entry:

In this exercise, you will learn how to enter simple schematic and run a simulation to perform timing simulation of an inverter designed using gpdK090 technology.

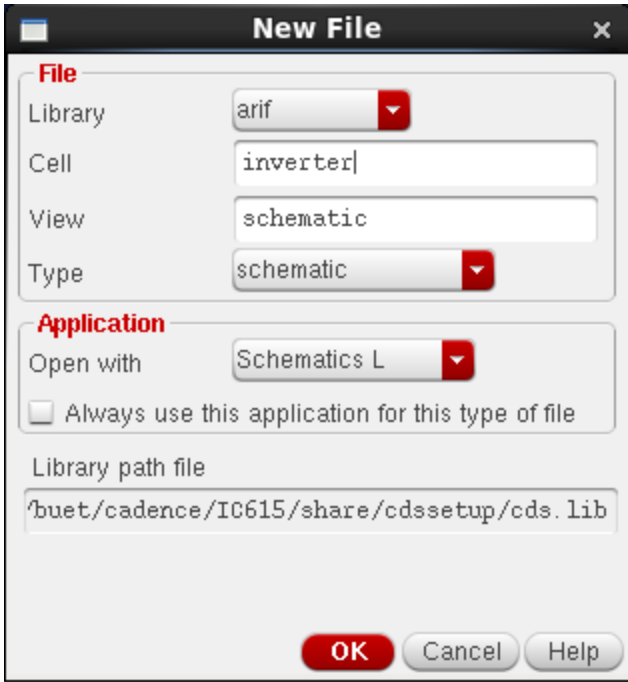
1. In the **CIW**, execute **File > New > Cellview**. Set up the ‘**New File**’ form as follows:
Library: mylib, **Cell:** inverter, **View:** schematic, **Type:** schematic, **Open with:** Schematics L;
then click **OK**.




2. This blank window shall now appear.

Instance Creation:

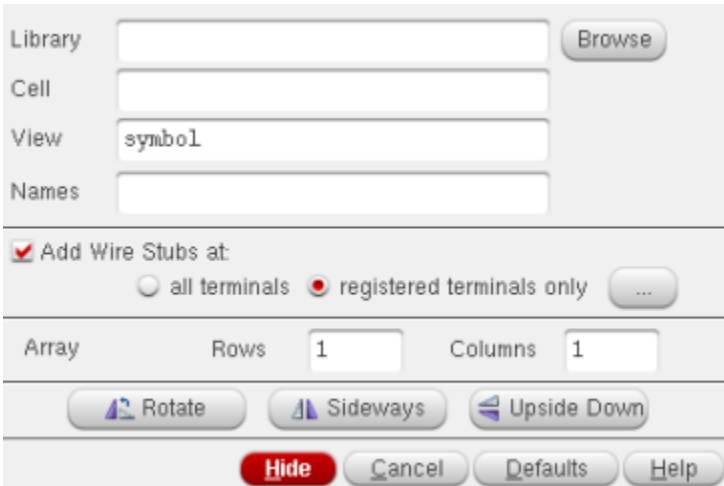1. To create an instance, you can execute **Create > Instance** in Virtuoso schematic editor window or simply use shortcut key “i”. The following window will appear:



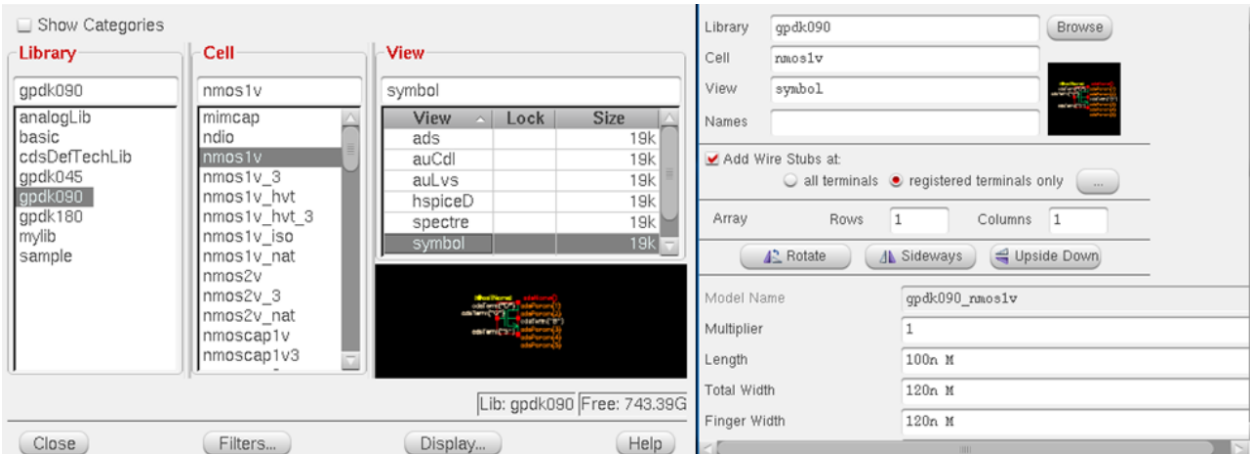2. Click **Browse** to select a library component. Another window will show up. Choose **Library:** gpd090, **Cell:** nmos1v, **View:** symbol. (Note that while you are doing this, the ‘Add Instance’ form is getting updated as well).



3. Make sure that the view name field in the form is set to symbol. After you complete the form, move your cursor to the schematic window and click left button of mouse to place the

component. After entering the components, click Cancel in the Create Instance form or press Esc keeping your cursor in the schematic window.




Similarly, add pmos1v cell. If you place component in the wrong location, press ‘m’ on keyboard, click once on the component to select it and move the mouse to move the component to your desired location.

4. Now we can adjust the sizes of the transistors by editing instance properties. Left click on the NMOS to select the component. Then, press “q” to modify its properties, or in schematic editor window, execute **Edit > Properties > Object**. You will update the Library Name, Cell Name, and the property values given in the table below as you place each component. The inverter design contains the following cells from the following libraries.

Library Name	Cell Name	Properties/Comment
gpdk090	nmos1v	For NM0, Width=240n (this is 2x the minimum channel width)
gpdk090	pmos1v	For PM0, Width=480n
analogLib	vdd	
analogLib	gnd	

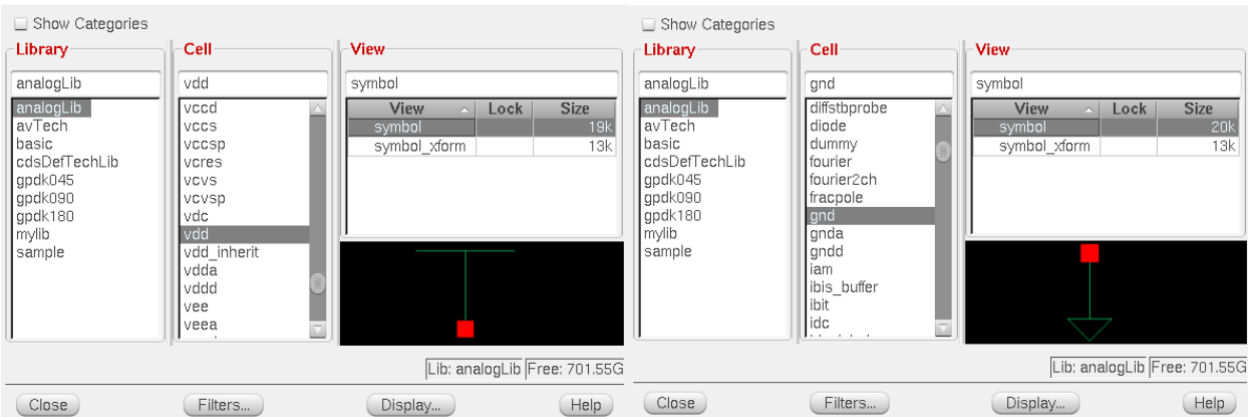
For example, while modifying the transistor width for NMOS, set **Total Width** to 240n, and then press ‘Tab’ key and the **Finger Width** will be set to the same value. Click **OK**. Repeat this for PMOS to set **Total Width** and **Finger Width** to 480n. To deselect any object, press keyboard command “Ctrl+d”. Next, instantiate power nets (cell **vdd** and **gnd** from **analogLib** library).



5. Execute **Create > Pin** or press ‘p’ on keyboard. ‘Add Pin’ form will appear. Enter the name of the pin and **Direction** of the pin. Add all the pins (**in**, **out**) to the schematic. For an inverter, gate input pin (e.g., in) is the input and output pin (e.g., out) at the common node between drains of NMOS and PMOS is output of the inverter. So, select **Direction** property as **input** for **in**, and **output** for **out**.

Pin Names	in	Pin Names	out
Direction	input	Direction	output
Usage	schematic	Usage	schematic
Signal Type	signal	Signal Type	signal
Attach Net Expression:	No	Attach Net Expression:	No
Property Name		Property Name	
Default Net Name		Default Net Name	
Font Height	0.0625	Font Height	0.0625
Font Style	stick	Font Style	stick
Rotate	Sideways	Rotate	Sideways
Upside Down	Show Sensitivity >>	Upside Down	Show Sensitivity >>
Hide	Cancel	Hide	Cancel
Defaults	Help	Defaults	Help

 6. Use **Add > Wire** menu or simply press ‘w’ key while staying on the schematic editor to enter wiring mode / Esc to exit. Click and release left button of mouse to start wire connections and click again at another point to draw wire connection. It is a good practice to periodically save your work by clicking on **Check and Save** button (the checkmark button just below the Tools menu). You can also save your work from the drop-down menu **File > Save**. The final schematic looks like the following one:




7. Click **Check and Save**.
8. Check CIW for errors or warnings. Some license warnings may be ignored. If there are no error or design warning, you should see the following message:


```
INFO (SCH-1170): Extracting "inverter schematic"
INFO (SCH-1426): Schematic check completed with no errors.
INFO (SCH-1181): "mylib inverter schematic" saved.
```


Netlist and Simulation:

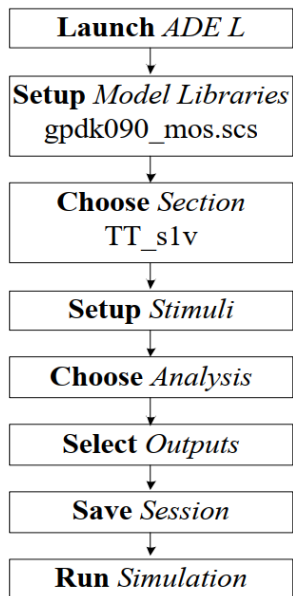The following flowchart shows the steps to be executed to simulate a design using ADE L:



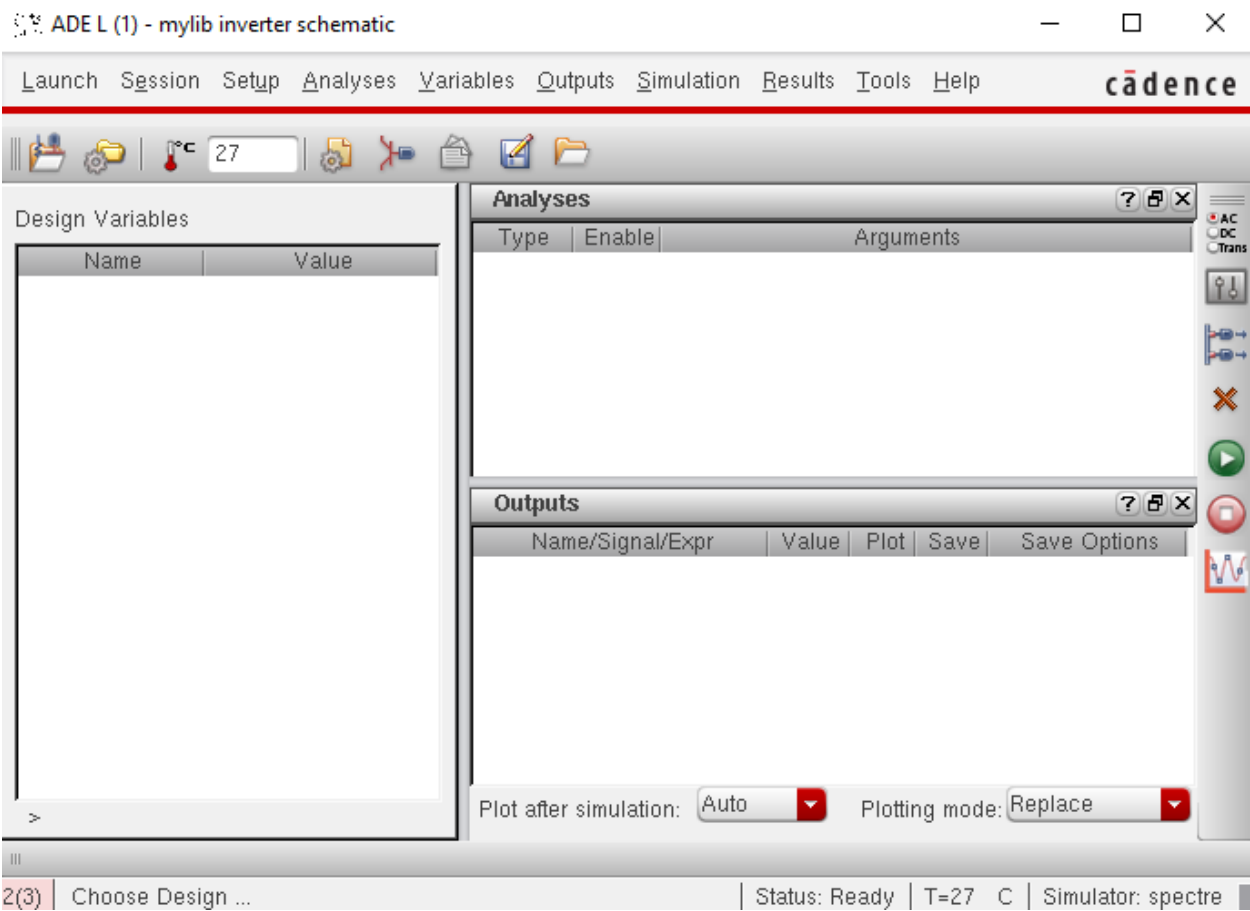1. In the Schematic editor window, execute **Launch > ADE L**. The **Analog Design Environment (ADE) L** window will arrive.




2. Set up the model libraries by executing **Setup > Model Libraries**. ‘**Model Library Setup**’ Window will appear:



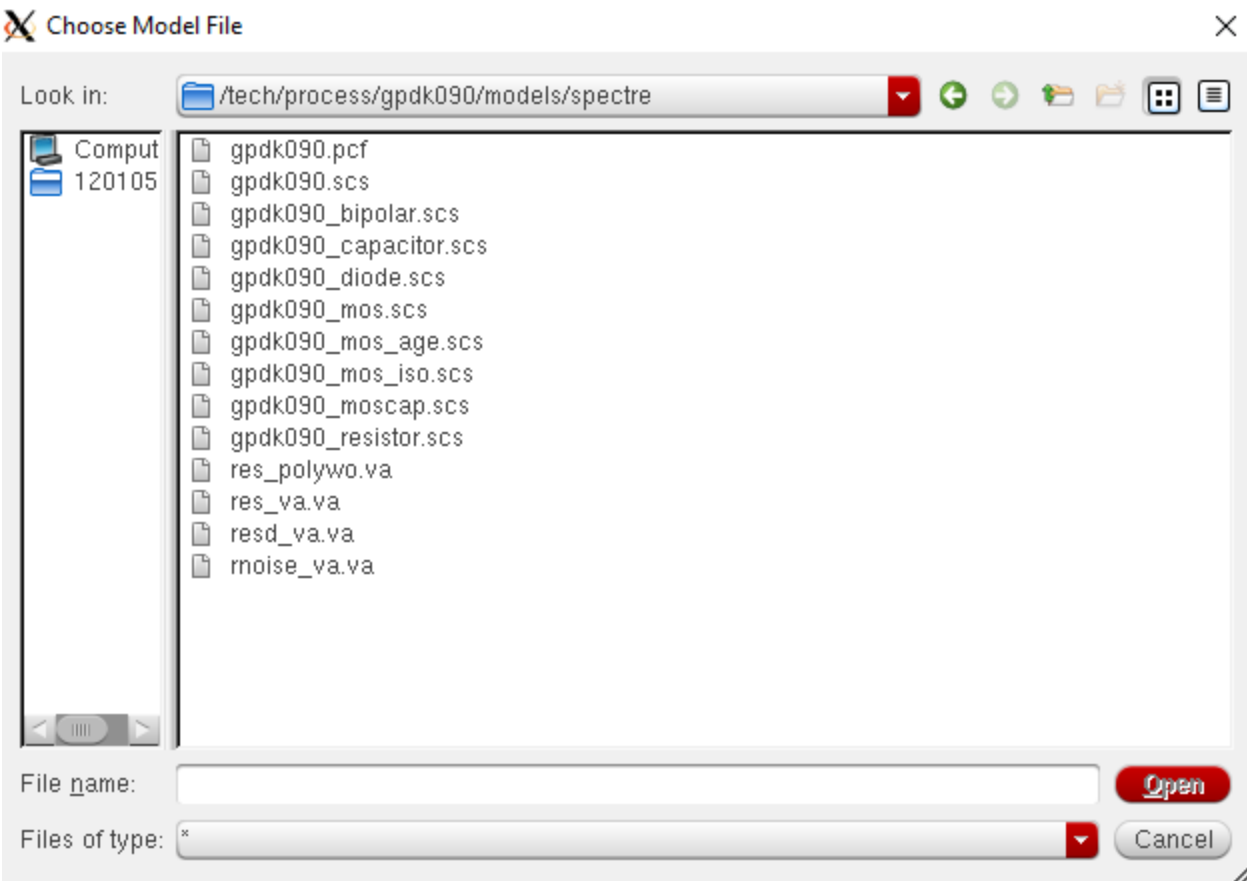
3. Click twice on the file name given under **Global Model Files**. An ash-colored button will appear.



Click on the button. ‘**Choose Model File**’ window will appear.



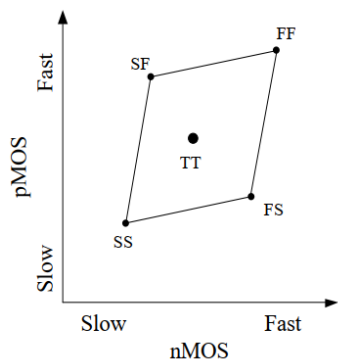
4. Select **gpdk090_mos.scs** from the list. Click **Open**.
In this model file, there are models to simulate various corners like fast-fast (FF), fast-slow (FS), typical-typical (TT) etc. These are called process corners, depending on the speed of MOS transistors (NMOS and PMOS). Refer to the following figure for the definition of process corners:




We will choose the section typical from the **Section** scroll bar and select the section '**TT_s1v**'. These will enable us to use the TT models of the 1.2 V MOS transistors. Only one **Global Model File** will be defined. Uncheck or delete any other model files that appear. Click **OK**.

Model File	Section
<input checked="" type="checkbox"/> /tech/process/gpdk090/models/spectre/gpdk090_mos.scs	TT_s1v
<input type="checkbox"/> <Click here to add model file>	

 
5. Now execute **Setup > Stimuli** to assign signals to pins of the inverter.



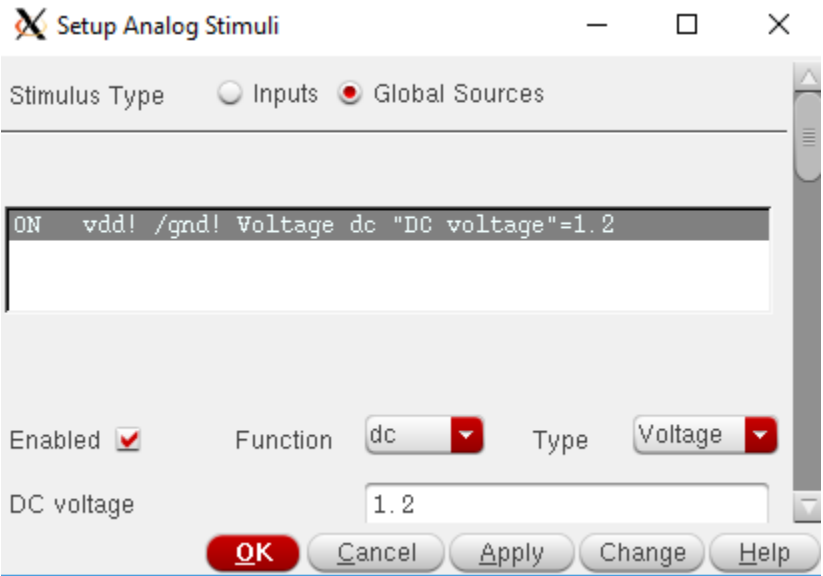
6. In ‘Setup Analog Stimuli’ window, select Global Sources. Now you can see global power net **vdd!**. Click on **Enabled**, Select **dc** under **Function** and **Voltage** under **Type**. Put a value of 1.2 on the **DC voltage** box. The filled-up form for ‘vdd!’ will look like the one below. Click **Apply** (clicking **OK** will close the window and it will have to be reopened to setup inputs).



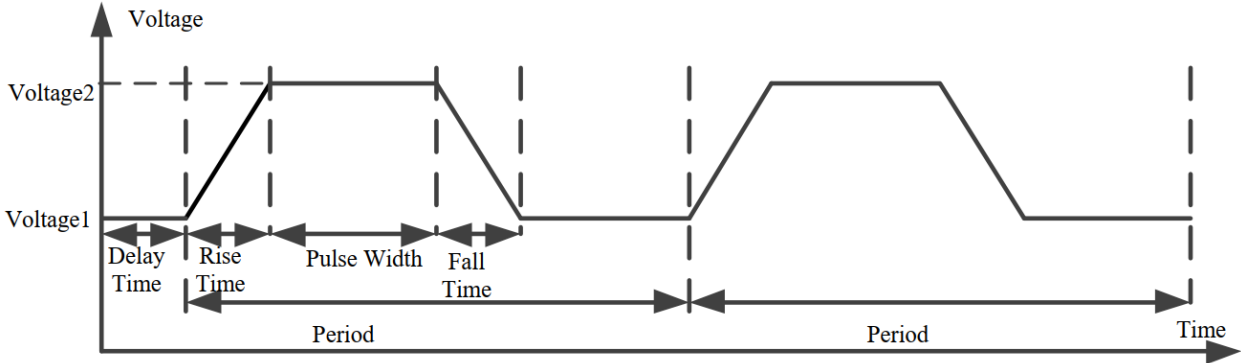
7. Select **Inputs**. For input pin ‘in’, we have to set a pulse waveform. The following figure shows the definition of pulse parameters:




For setting signal to input pin ‘in’, select **Inputs** in **Setup Analog Stimuli** window. Click on ‘**Enabled**’, select **Function**: ‘pulse’, **Type**: ‘Voltage’. Parameters for pulse source will be as follows: **Voltage1** = 0V, **Voltage2** = 1.2V, **Period** = 40n, **Delay time** = 3n, **Rise time** = 3n, **Fall time** = 3n, **Pulse width** = 20n. Click **Apply** and then click **OK**. (**Delay**, **Rise time** and **Fall time** can also be set at ps ranges for sharp transitions).

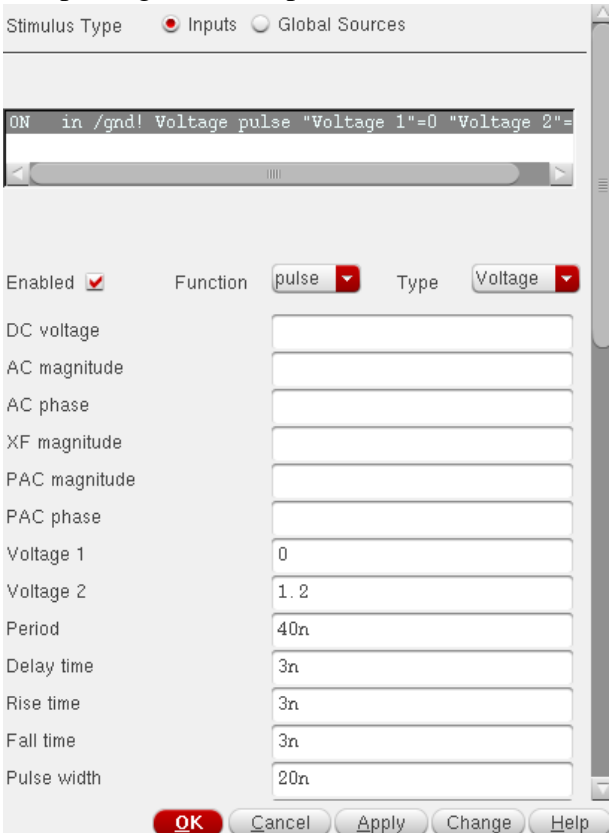

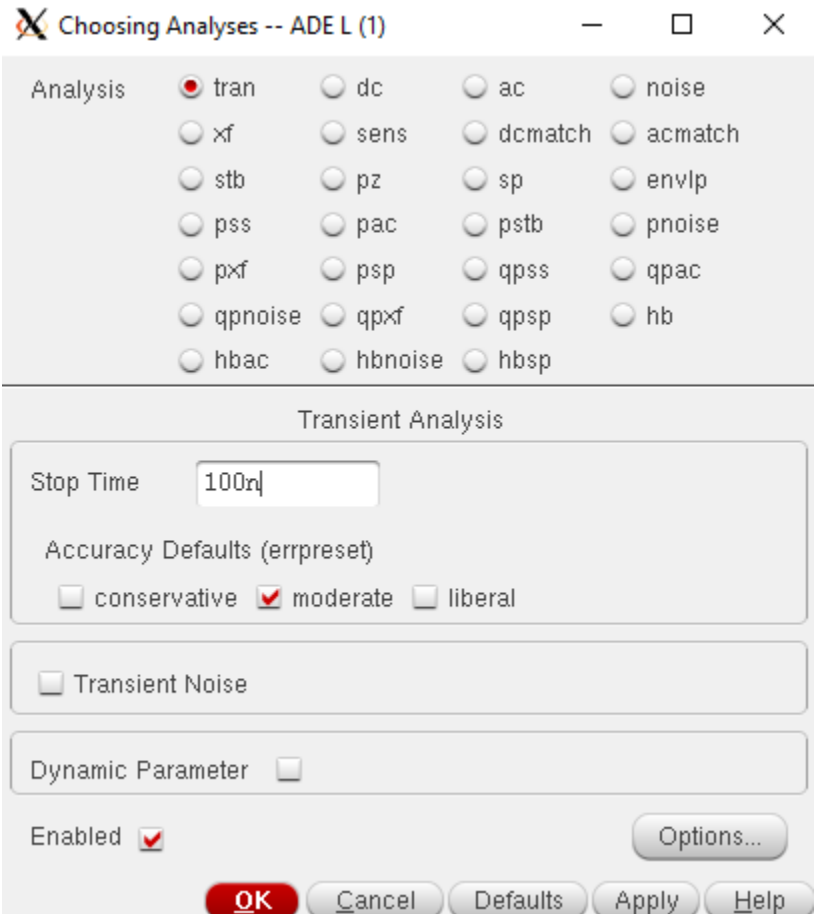
8. Now choose the analysis to be done from **Analyses > Choose**. Select transient (**tran**) analysis to be done. Provide a reasonable value for ‘stop time’ to observe few periods of signals. (e.g., **Analysis: tran, Stop Time: 100n, Accuracy Defaults: moderate**). Click **OK**.



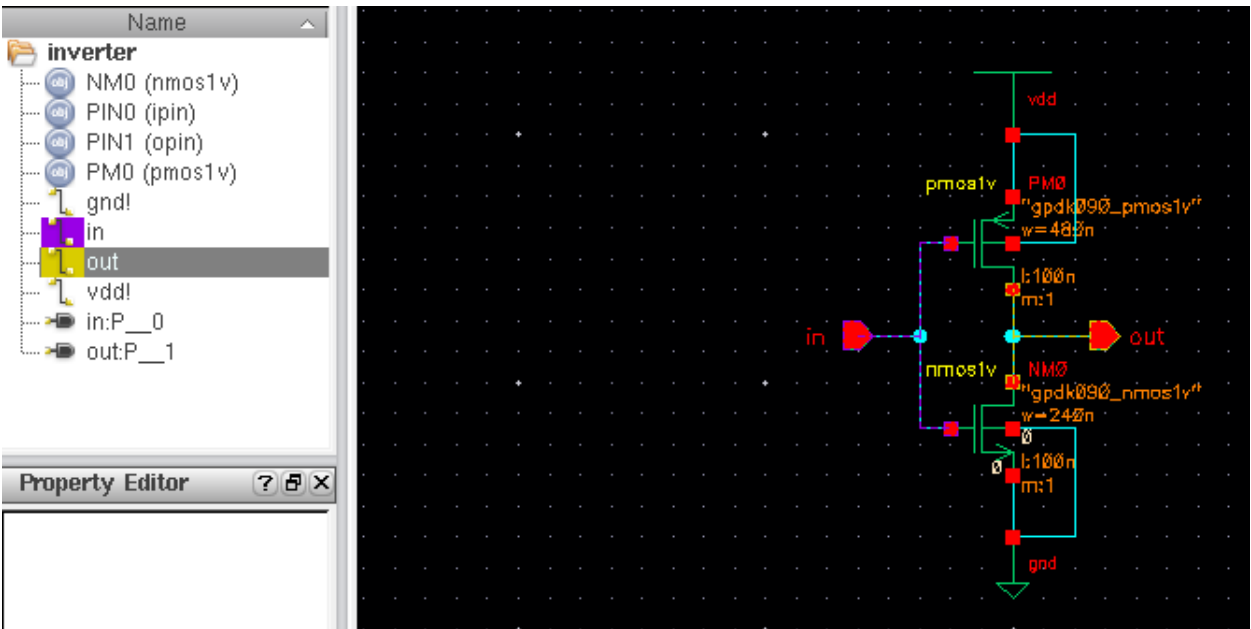
9. Select the output to be plotted by executing **Outputs > To be plotted > Select on Design** in the ADE window. Schematic editor window will pop up, select ‘out’ and ‘in’ by clicking on the pins/terminals or selecting from the list on the left-hand side as shown in the figure below. When you select them, you will see colors being assigned to these pins.



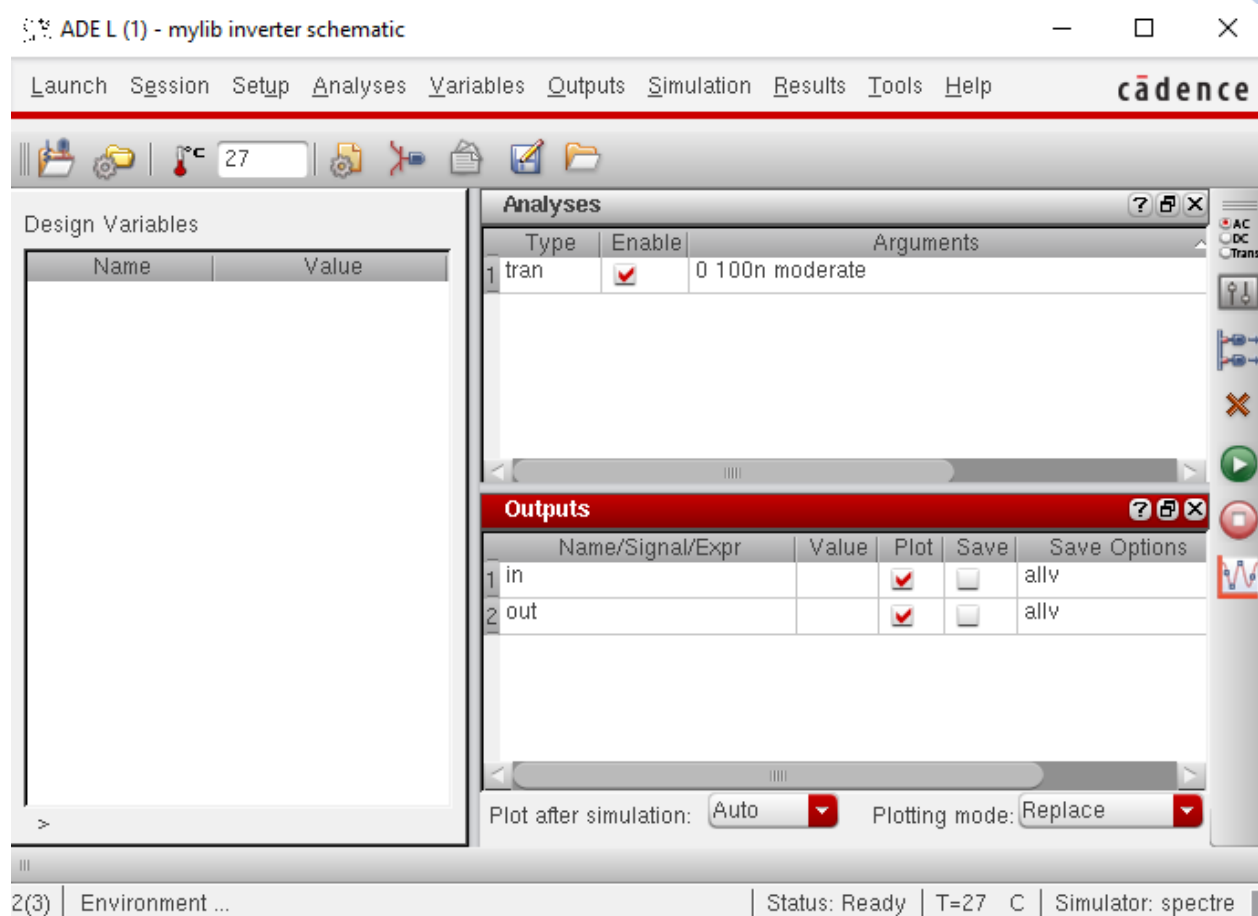
10. Your Analog Design Environment window should now look like the following:



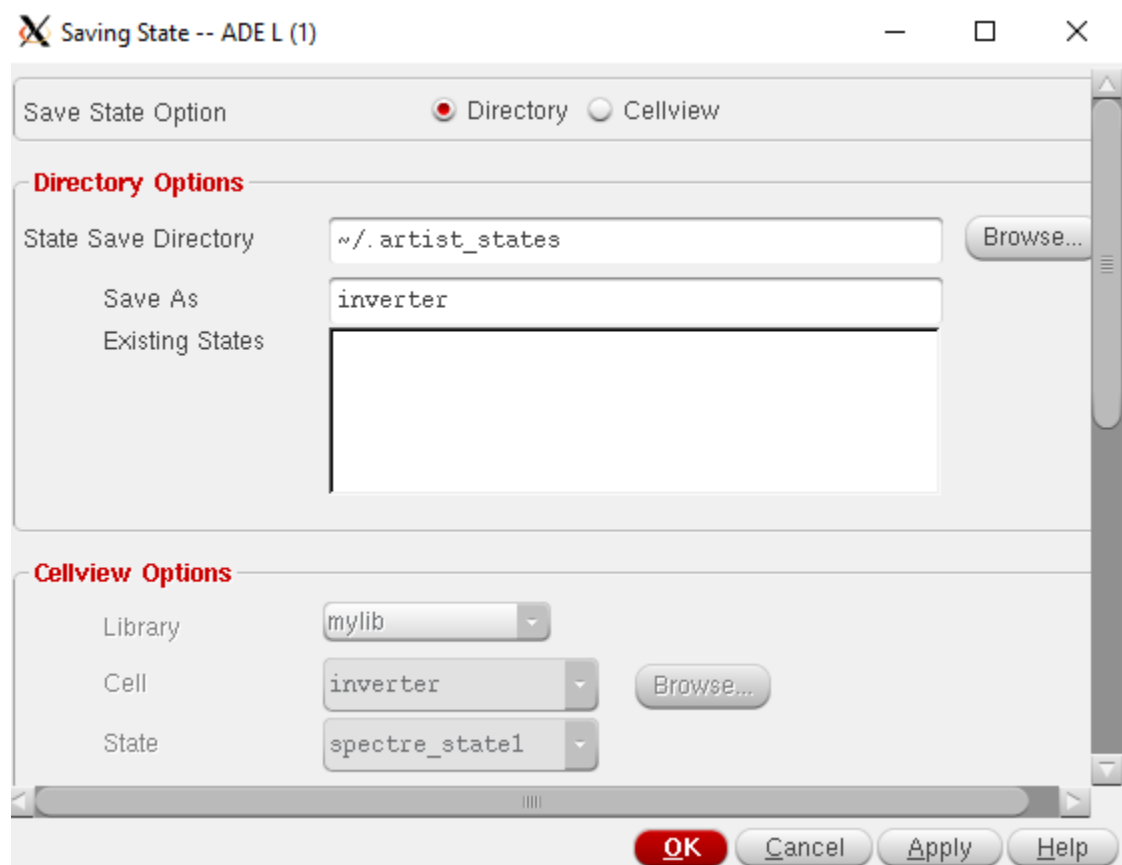11. Before closing the Virtuoso Analog Design Environment window, it is a good idea to save design settings in a state file, so we can load it up next time. To do this, execute **Session > Save State** and save state name in the 'Save As' field as 'inverter'. Next time you run Cadence, you can simply load the simulation settings from this file by executing **Session > Load State**.



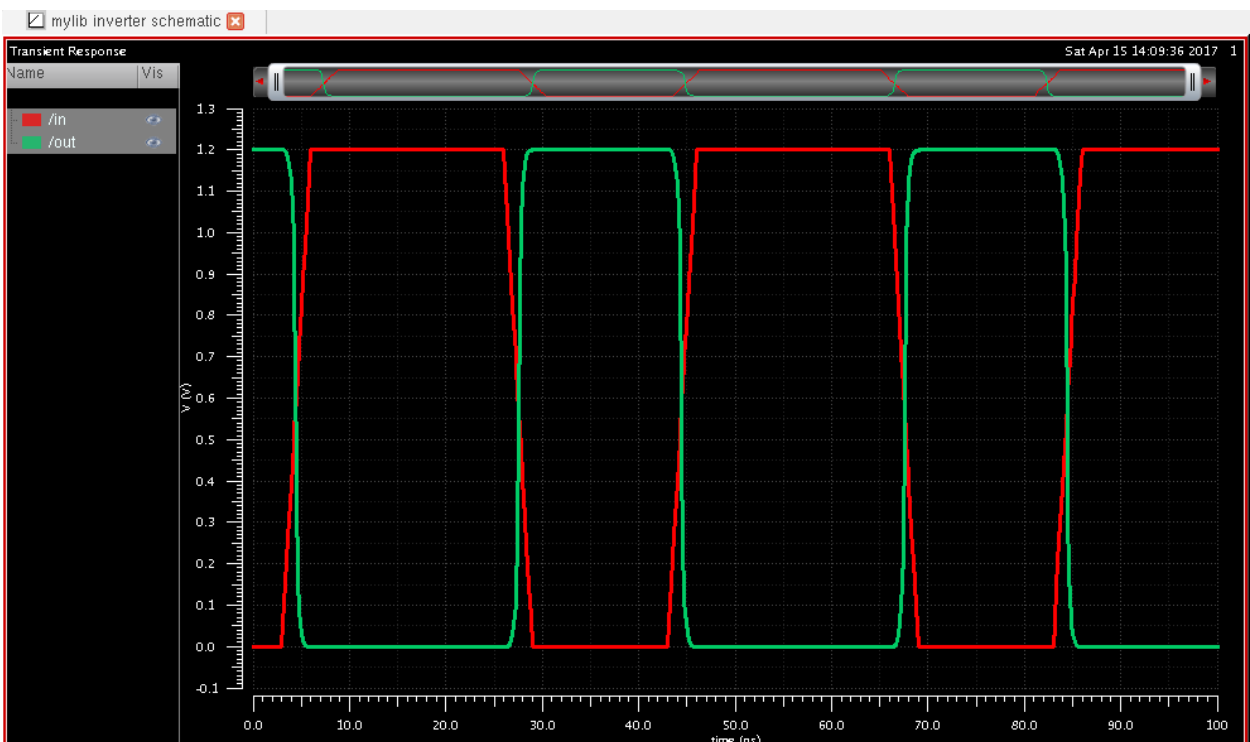
12. Now run the simulation by executing **Simulation > Netlist and Run** in the ADE window. The simulation will run and the output will appear in Virtuoso Visualization & Analysis XL window as shown below.



 13. Finally, we are going to separate the plots into two sub-graphs. Click on the following icon for splitting graphs.




The final plot should look like the one shown below:



Definitions:

 Three main timing parameters are associated with CMOS devices – rise time, fall time, and propagation delay. Most often, in discussion with regard to these parameters, the system response of an inverter is used. The following figure defines rise time, fall time and propagation delay of a gate with the example of an inverter:




Referring to the above figure, rise time is the time that it takes to charge the output capacitive load. Fall time is the time it takes for the output capacitive load to discharge. The rise and fall time are usually measured from 10% to 90% and from 90% to 10% of the steady state value of a waveform, respectively.

Propagation delay is the time difference between approximately 50% of the input transition and approximately 50% of the output transition.


Measurement:

Waveform calculator can be used to perform many different measurements and transformations on the waveforms displayed in the waveform window. This includes – computing the average of a waveform (e.g., power) over the entire length of the simulation or in a given period of time, finding the propagation delay of between input and output signals, or addition / subtraction / multiplication / division of waveforms, etc.

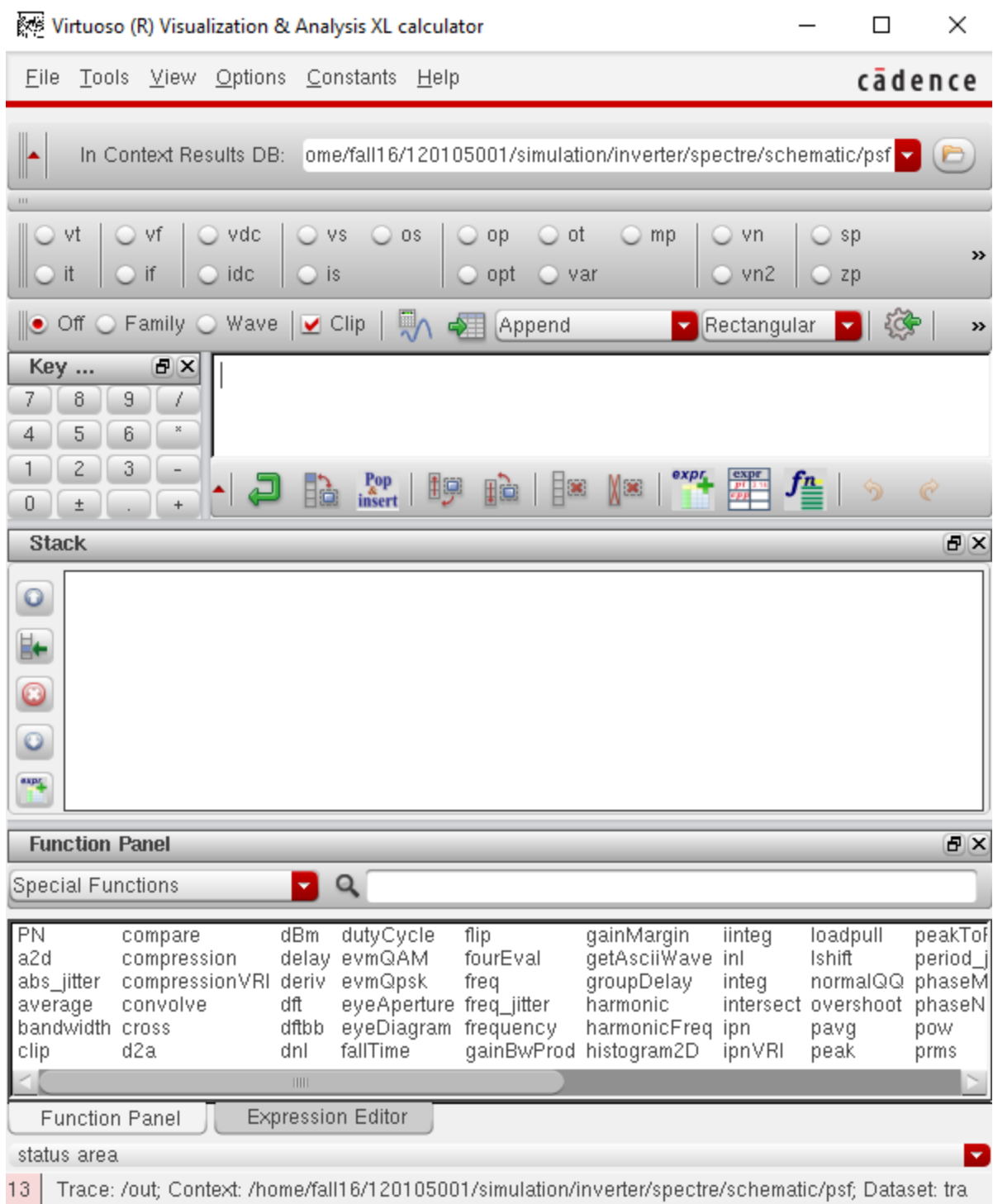1. Execute **Tools > Calculator** in Virtuoso Visualization & Analysis XL window. ‘**Virtuoso Visualization & Analysis XL calculator**’ window will pop-up:



 2. Select ‘vt’. Go to Schematic editor window and click on input node ‘in’. An expression (e.g., VT(“in”)) will appear. Copy the expression.



3. In the **Function Panel**, select ‘Special functions’ and select ‘delay’.



4. The following window will appear. Put the expression previously obtained in the field ‘Signal1’. Do the same for output signal ‘out’ to fill in the field ‘Signal2’.

Fill up the rest as follows:

5. Click **OK**. The following expression should appear:

6. Click on Evaluate the buffer icon.



The propagation delay (in seconds) will be displayed in the window.

Waveform Calculation:

1. Open the ‘delay’ function window under **Waveform calculator** in the same way that you followed for propagation delay measurement. This time both **Signal1** and **Signal2** will be **VT("/out")**.

- Example: Rise time calculation of rising edge 2 for an inverter:

delay

Signal1	<input out")"="" type="text" value="VT("/>				
Signal2	<input out")"="" type="text" value="VT("/>				
Threshold Value 1	<input type="text" value="0.12"/>	Threshold Value 2	<input type="text" value="1.08"/>		
Edge Number 1	<input type="text" value="2"/>	Edge Number 2	<input type="text" value="2"/>		
Edge Type 1	<input type="text" value="rising"/>		Edge Type 2	<input type="text" value="rising"/>	
Periodicity 1	<input type="text" value="1"/>	Periodicity 2	<input type="text" value="1"/>		
Number of occurrences	<input type="text" value="single"/>		Plot/print vs.	<input type="text" value="trigger"/>	
Start 1	<input type="text" value="0.0"/>	Start 2 relative to	<input type="text" value="trigger"/>		


-
- The screenshot shows the TI-84 Plus CE calculator interface. The 'Append' menu is open, with 'Rectangular' selected. The 'Key' field displays '709.9E-12'. The bottom toolbar includes icons for 'Pop insert', 'expr', and 'fn'.

Save Options


Select signals to output (save) ☐ none ☐ selected ☐ lvlpub ☐ lvl ☒ allpub ☐ all

Select power signals to output (pwr) ☐ none ☐ total ☐ devices ☐ subckts ☒ all

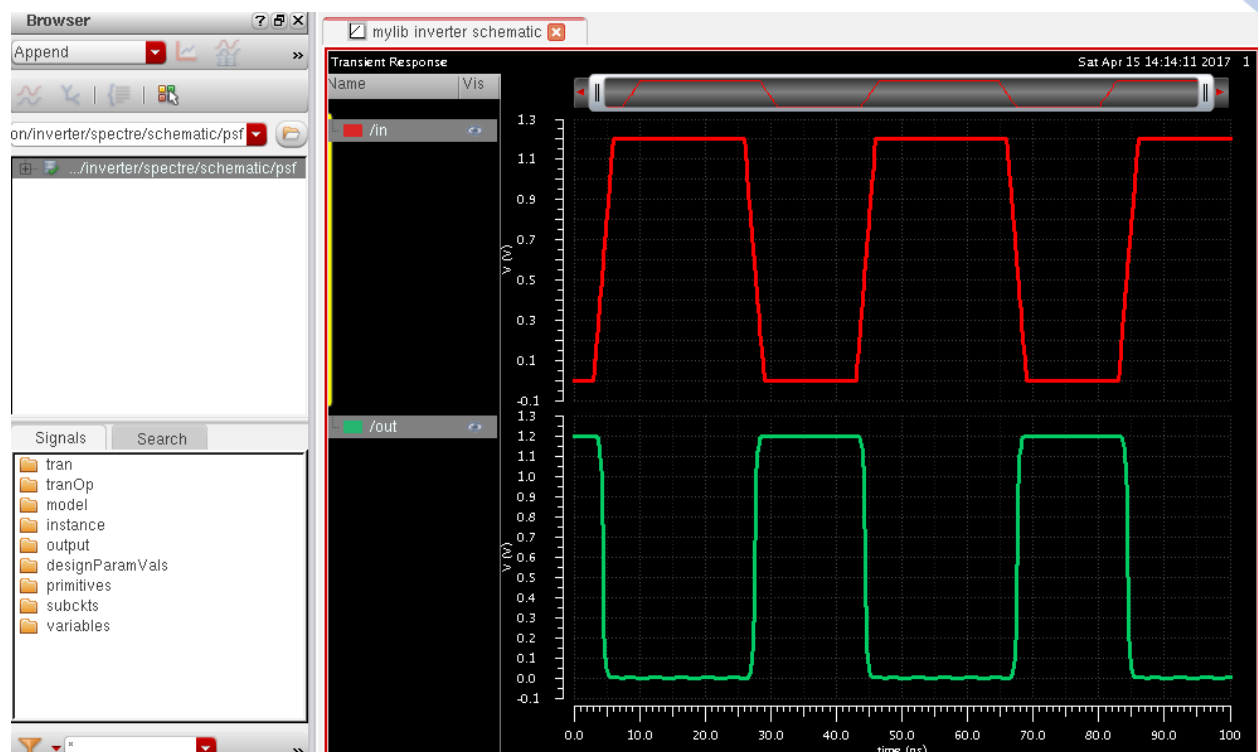
2. Then simulate the circuit as usual, by executing Simulation > Netlist and Run. Execute Tools > Result Browser in ADE L window. ‘Result Browser’ window will appear on the left side in ‘Virtuoso Analysis and Visualization XL’ window.



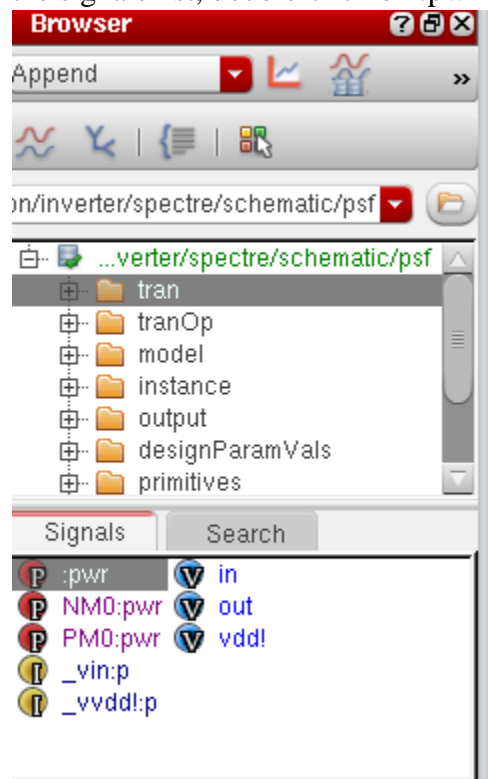3. Double-click on tran. From the signals list, double-click on :pwr



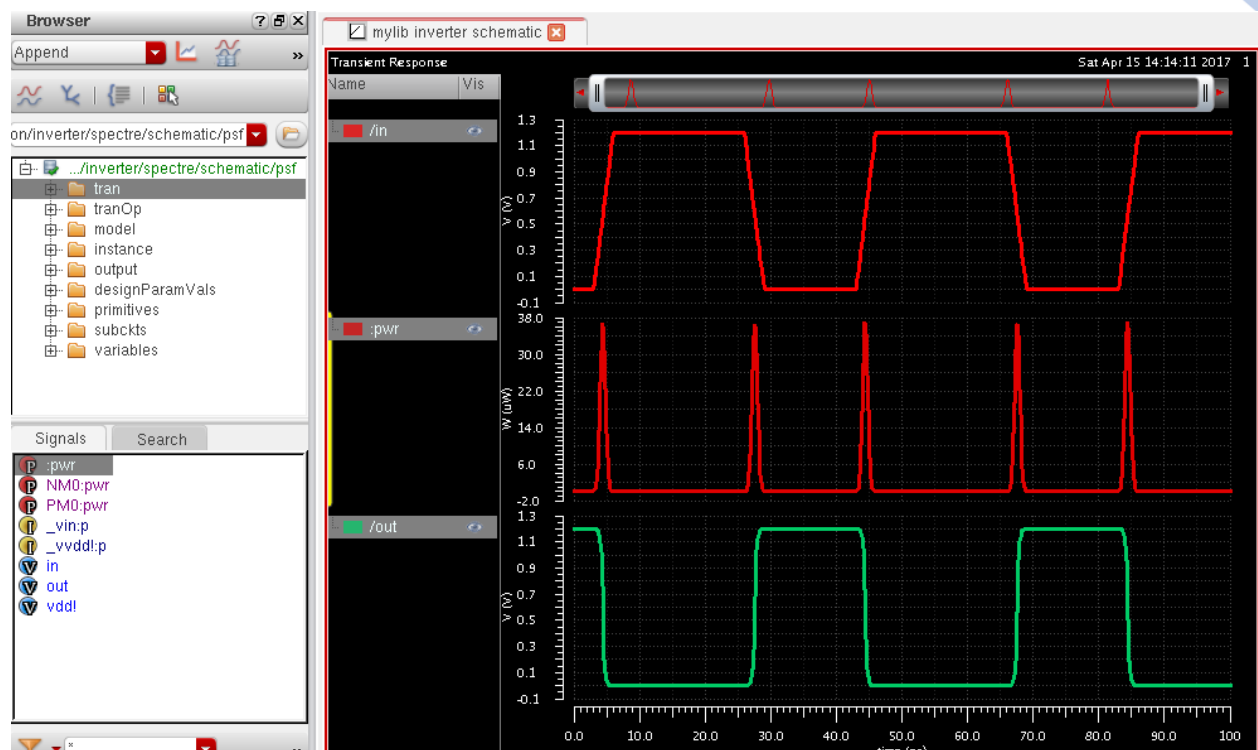
4. The waveform display window will show the “:pwr” (the instantaneous power consumed by the whole circuit) along with ‘in’ and ‘out’ signals.



5. Now, open Waveform calculator window. The calculator window appears. Make sure the “Wave” and “Clip” options are selected.



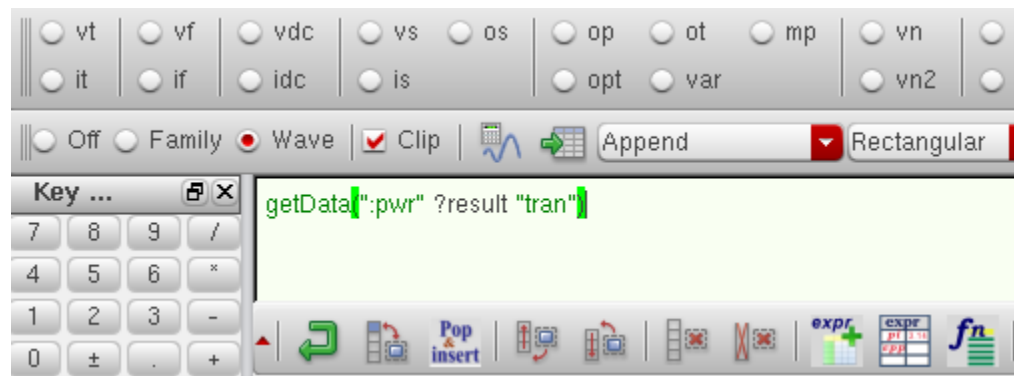
6. Now switch back to the waveform window and left click the mouse once on the power waveform. Then switch back to the calculator window. The buffer window should be filled in as follows:



7. Now select ‘average’ from ‘Special Functions’ Menu.



 8. The buffer will now look like the following one:



9. Click on Evaluate the buffer icon and the average power dissipation in that time window will be displayed (about 1.838 μ W in this example).



Rubrics:

Criteria	Below Average (1)	Average (2)	Good (3)
Formatting	Report is not properly formatted, missing objectives, discussions, and references.	Report is somewhat formatted but missing proper references.	Report is properly formatted.
Design	Design steps are somewhat followed, and results have errors.	Design steps are properly followed, and the results are flawless.	
Writing	Writing is poor and not informative. It does not address the design decisions and contains high plagiarism.	Writing is average and original. Design decisions are somewhat explored.	Writing is excellent with every design decision adequately explored.
Diagram	Diagrams are of bad quality and unreadable.	Diagrams are clear and of high quality.	